

CALIFORNIA STATE UNIVERSITY FULLERTON

EGEE 435 Project 3 Report


Submitted by: Mayank Pathak

CWID: 89330183

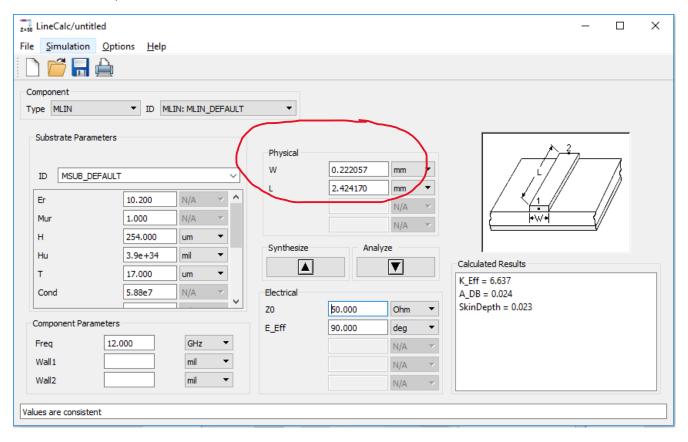1. Calculate the device's dimension


Using the LineCalc tool in ADS, we get the following results

For Zo = 50 ohms, the device dimension are encircled as below





For Zo = 50 / Squareroot of 2 = 35.35

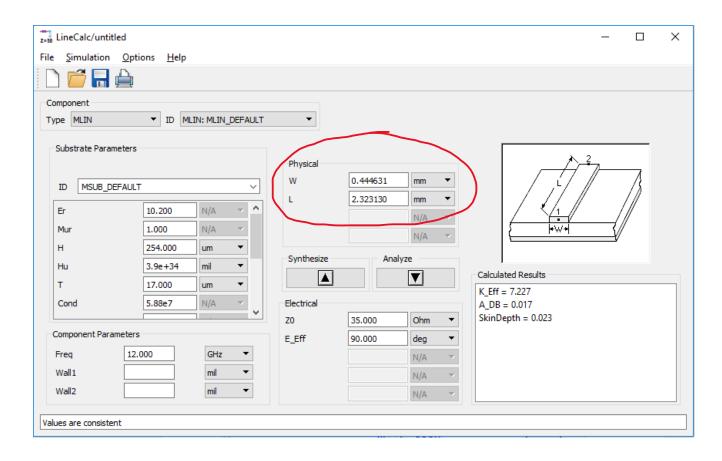Therefore rounding off Zo = 35 Ohms, the device dimension are encircled as below



2. Run Simulation using ADS Software

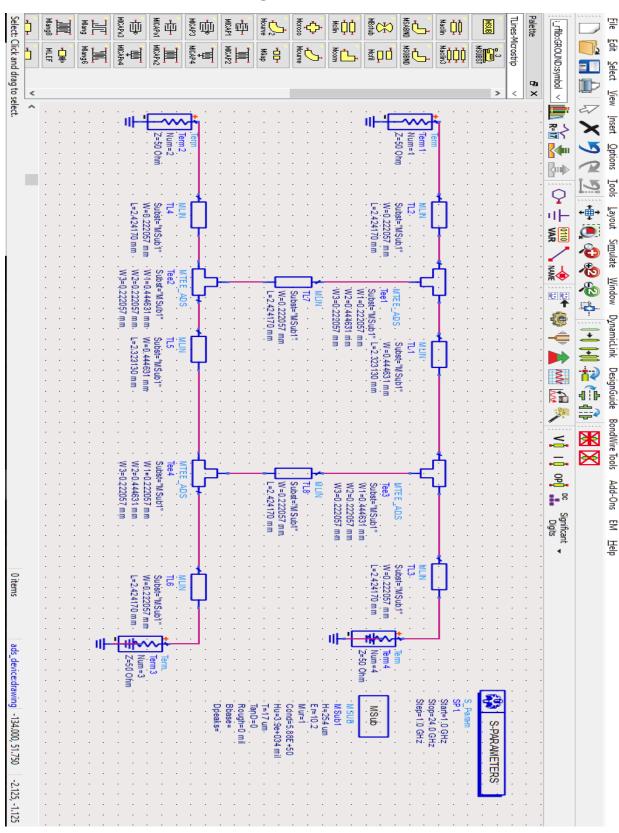

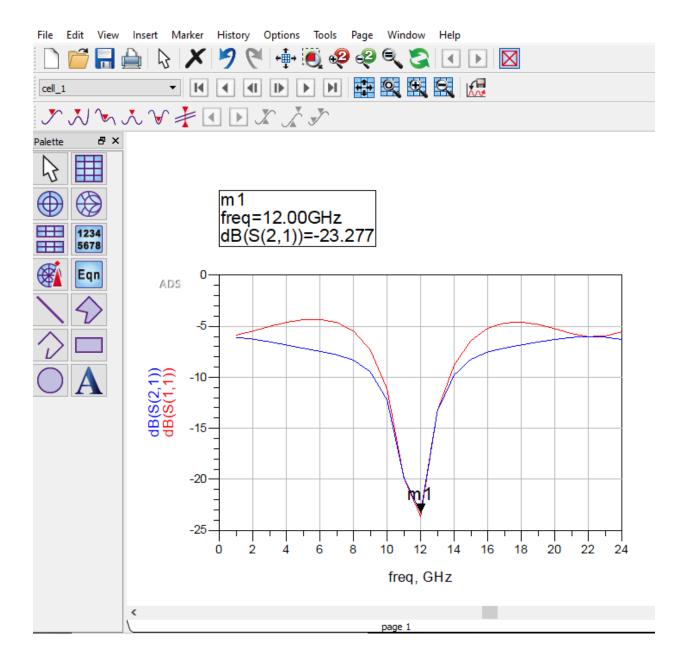

Plot Layout:

